

**B.Tech 3rd Semester Exam., 2020  
(New Course)**

**DIGITAL ELECTRONICS**

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Choose the correct answer of the following  
(any seven) : 2×7=14
- (a) Dynamic RAM employs
    - (i) capacitor or MOSFET
    - (ii) FET or JFET
    - (iii) capacitor or BJT
    - (iv) BJT or MOS
  - (b) The resolution of a 10-bit AD converter for an input range of 10 V is approximately
    - (i) 1 V
    - (ii) 1 mV
    - (iii) 10 mV
    - (iv) 100 mV

- (c) The evolution of PLD begins with
  - (i) EROM
  - (ii) RAM
  - (iii) PROM
  - (iv) EEPROM
- (d) The parameter through which 16 distinct values can be represented is known as
  - (i) bit
  - (ii) byte
  - (iii) word
  - (iv) nibble
- (e) The number of full and half adders required to add 16-bit number is
  - (i) 8 HA, 8 FA
  - (ii) 1 HA, 15 FA
  - (iii) 16 HA, 0 FA
  - (iv) 4 HA, 12 FA
- (f) If we record any music in any recorder, such type of process is called
  - (i) multiplexing
  - (ii) encoding
  - (iii) decoding
  - (iv) demultiplexing

(g) The no. of D flip-flop required to form a 5-bit ring counter is

- (i) 3  
 (ii) 4  
 (iii) 5 ✓  
 (iv) None of the above

(h) An overflow is a/an

- (i) hardware problem  
 (ii) software problem ✓  
 (iii) user-input problem  
 (iv) input-output problem ✓

(i) The systematic reduction of logic circuits is accomplished by

- (i) symbolic reduction  
 (ii) TTL logic ✓  
 (iii) Boolean algebra ✓  
 (iv) truth table

(j) A latch is an example of a/an

- (i) monostable multivibrator  
 (ii) astable multivibrator  
 (iii) bistable multivibrator ✓  
 (iv) 555 timer ✓

2. (a) Design an excess-3 to BCD code converter using minimum number of NAND gates. 8

1. (a) Prove the following : 3×2=6

$$(i) A \oplus B = \bar{A} \oplus \bar{B}$$

$$(ii) A \oplus \bar{B} = A \oplus B = \bar{A} \oplus B$$

2. (a) How can we implement preset and clear inputs in a flip-flop? Explain with the help of a diagram and list their uses. 3+3=6

(b) Design a Mod 9 counter using 7 flip-flops. 8

3. (a) Explain internal organization of 16×2 memory chips using suitable diagrams. Calculate the maximum rate at which data can be stored and read for a memory having following timing parameters : 4+2=6

Parameter	Time (ns)
Read to Output Valid Time ( $t_{RD}$ )	70
Data Setup Time ( $t_{DW}$ )	120
Read to Cycle Time ( $t_{RC}$ )	200
Write Release Time ( $t_{WR}$ )	0
Write Cycle ( $t_{WC}$ )	200

(b) Differentiate between Word Capacity and Word Size. Design a 16×8 CAM, using 8×2 CAM chips. 2+6=8

5. (a) Define resolution, linearity, accuracy and settling time of D/A converters. A typical D/A converter has a full-scale analog output of 10 V and accepts 6 binary bits as input. What will be the voltage corresponding to each analog step? 4+2=6

(b) Design a 3-bit parallel comparator A/D converter that provides output in 2's complement format. 8


6. (a) Design a BCD to 7-segment display decoder circuit using logic gates. 8

(b) Design full adder using the following : 3×2=6

(i) 8:1 mux

(ii) 4:1 mux

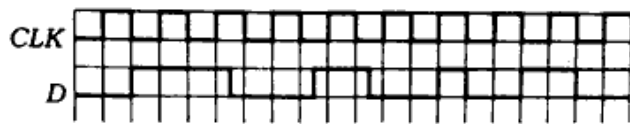7. (a) On the following graph, inputs CLK and D are shown :




They are inputs to a D latch and a positive edge triggered D flip-flop. Assuming initial output 0, draw the output waveform for flip-flop and latch. Do the two outputs differ? If so, why?

2+2+2=6

(b) Explain SIPO and SISO operations of shift register with relevant logic diagrams and truth tables. 8

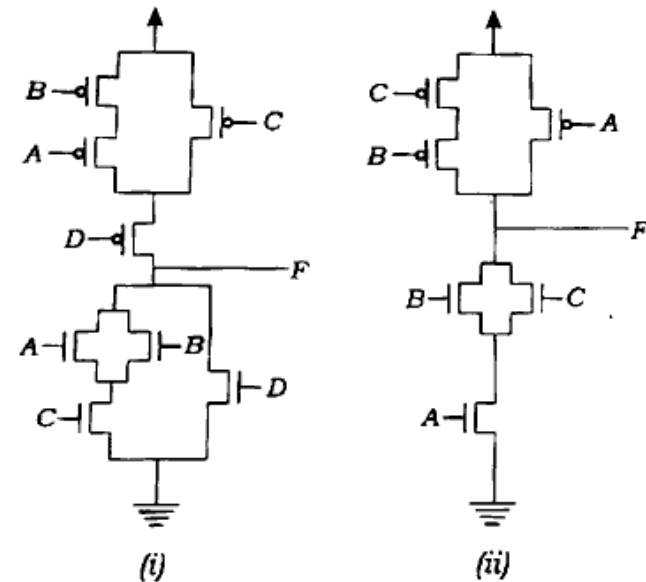8. (a) Identify the following logic functions implemented at F : 6



(b) Implement the following CMOS logics : 4×2=8

(i)  $\overline{AB(A+B)}$

(ii)  $\overline{((CD)+B)A}$

9. (a) What are weighted, non-weighted, cyclic and self-complementary codes? Explain each with examples. 8

✓(b) Find the values of  $X$  in the following conversions :  $2 \times 3 = 6$

✓(i)  $(95.10)_{10}$  to  $(X)_2$

✓(ii)  $(45.70)_8$  to  $(X)_2$

✓(iii)  $(168.16)_8$  to  $(X)_{16}$

\*\*\*