

Code : 031609

(2)

B.Tech 6th Semester Exam., 2019

POWER ELECTRONICS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **EIGHT** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer any seven of the following : $2 \times 7 = 14$

- (a) Draw the symbols of BJT, MOSFET and SITH.
- (b) The reverse recovery time of a diode is $t_{rr} = 3 \mu\text{s}$ and the rate of fall of the diode current is $di/dt = 30 \text{ A}/\mu\text{s}$. Determine the stored charge Q_{RR} in reverse recovery zone.
- (c) What is the softness factor of diodes?
- (d) Explain forward-biased safe operating area (FBSOA) of BJT.

(e) Define distortion factor (DF).

(f) A step-up d.c.-d.c. converter has input voltage $V_s = 10 \text{ V}$, inductance $L = 1 \text{ mH}$, duty ratio $d = 0.5$ and time period $T = 1 \text{ ms}$. Find the peak-to-peak ripple current in inductor.


(g) The H-bridge inverter has an $R-L-C$ load with $R = 10 \Omega$, $L = 31.5 \text{ mH}$ and $C = 112 \mu\text{F}$. The inverter frequency is $f_o = 60 \text{ Hz}$ and d.c. input voltage is $V_s = 220 \text{ V}$. Find the output fundamental r.m.s. voltage.

(h) Find the line-to-line r.m.s. voltage of three-phase inverter operating in 180° conduction mode if d.c. input voltage $V_s = 220 \text{ V}$.

(i) Explain dynamic current sharing in parallel operation of thyristors.

(j) The full converter is connected to a 120 V , 60 Hz supply. The load current $I_a = 8 \text{ A}$ is continuous and its ripple content is negligible. If the delay angle is $\alpha = \pi/3$, calculate power factor.

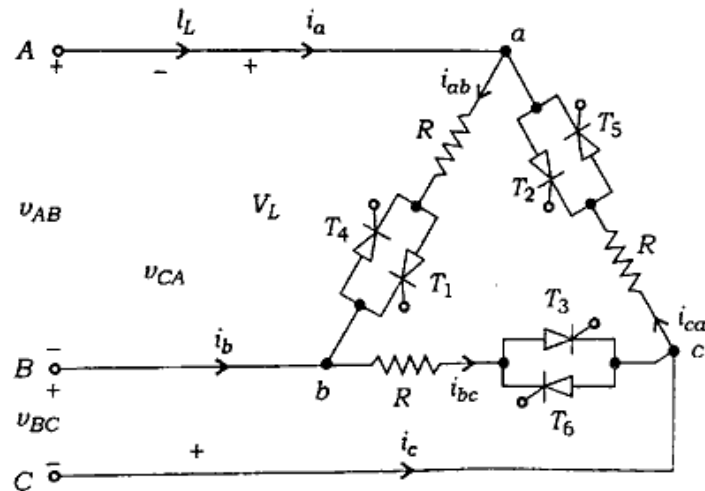
2. (a) The three-phase bidirectional delta-connected controller shown in the figure below has a resistive load of $R = 10 \text{ ohm}$. The line-to-line voltage is $V_s = 208 \text{ V}$ (r.m.s.), 60 Hz and the delay angle is $\alpha = 2\pi/3$. Determine the r.m.s. output voltage V_o , the input PF and the r.m.s. current of a thyristor I_R :



- (b) Explain three-phase full-wave delta-connected controller with various waveforms.

14

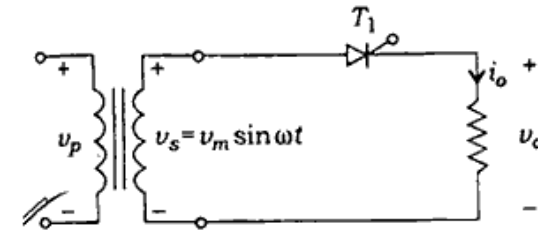3. (a) A single-phase half-wave converter shown in the figure below is operated from a 120 V, 60 Hz supply and the resistive load is $R = 10 \Omega$. If the average output voltage is 50% of the maximum possible output voltage, calculate the delay angle, the r.m.s. and average output currents :



- (b) Explain three-phase full converter with R-L load with various waveforms.

14


4. (a) Explain two-transistor model of a thyristor.

- (b) A single-phase half-bridge inverter has resistive load of $R = 5 \Omega$ and the d.c. input voltage is $V_s = 100 \text{ V}$. Determine the r.m.s. output voltage at the fundamental frequency V_{01} and the output power P_o .

14


5. (a) A single-phase full-bridge inverter is operated at 1 kHz and uses a uniform PWM with four pulses per half-cycle for voltage control. Plot the fundamental component, distortion factor and THD against the modulation index M .

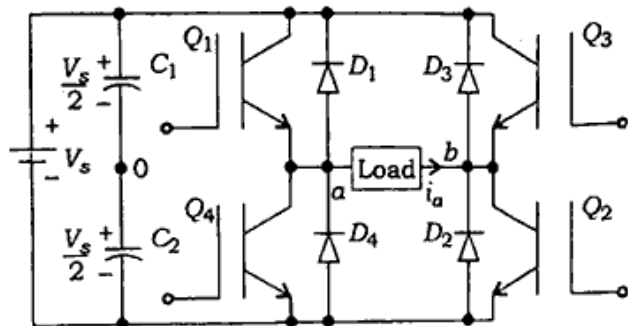- (b) The bridge inverter shown in the figure below has an $R-L-C$ load with $R = 10 \Omega$, $L = 31.5 \text{ mH}$ and $C = 112 \mu\text{F}$. The inverter frequency is $f_o = 60 \text{ Hz}$ and d.c. input voltage is $V_s = 220 \text{ V}$. Calculate the r.m.s. load current at the fundamental frequency I_{o1} and the THD of the load current :



14

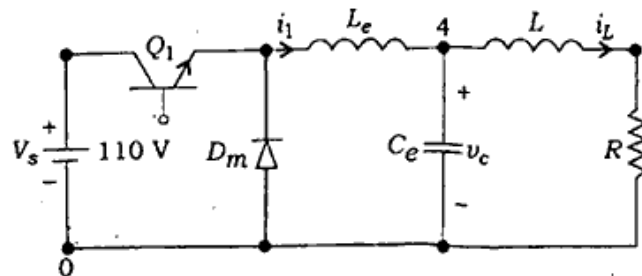6. (a) The buck converter shown in the figure below has a d.c. input voltage $V_s = 110 \text{ V}$, average load voltage $V_a = 80 \text{ V}$ and average load current $I_a = 15 \text{ A}$. The chopping frequency is $f = 10 \text{ kHz}$. The peak-to-peak ripples are 5% for load voltage, 2.5% for load current and 10% for filter L_e current. Determine the values of L_e , L , C_e :




- (b) Write on the steady state analysis of buck converter.

14

1. (a) Explain briefly about Cuk-converter.

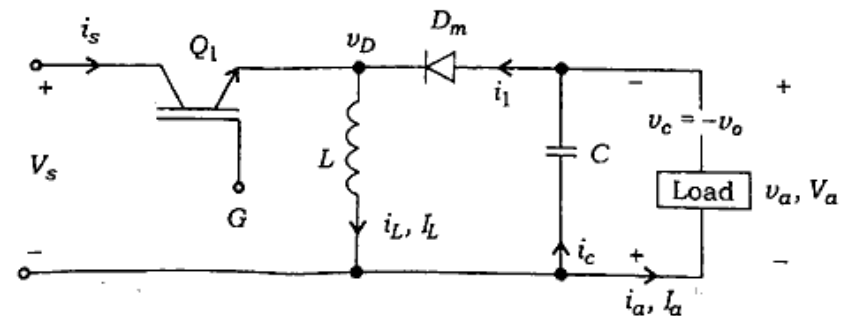- (b) The buck-boost regulator shown in the figure below has an input voltage of $V_s = 12 \text{ V}$. The duty cycle $k = 0.25$ and the switching frequency is 25 kHz . The inductance $L = 150 \mu\text{H}$ and filter capacitance $C = 220 \mu\text{F}$. The average load current $I_a = 1.25 \text{ A}$. Determine the peak-to-peak output voltage ripple ΔV_c and the peak-to-peak ripple current of inductor ΔI :



14

8. Write brief notes on any two of the following : 14

- (a) DC motor drive
- (b) AC motor drive
- (c) Modern PE devices
- (d) Commutation circuits ✓
