

N4008

1614408

2019(Even)

Time : 4Hrs.

Sem. IV - Che
E.E.E. Lab

Full Marks : 50

Pass Marks : 20

- 1.** Each question carries equal marks.
प्रत्येक प्रश्न का मान बराबर है।
- 2.** Perform any one experiment/study and furnish it report
किसी एक प्रयोग/अध्ययन को सम्पन्न करें एवं इसका पूर्ण प्रतिवेदन
तैयार करें।
- 3.** Experiment will be allotted through lottery to examinee/group
of examinees.
प्रयोग का आवंटन परीक्षार्थी/परीक्षाधियों के समूह को लॉटरी के ?
आधार पर किया जाएगा।
Necessary calculations, drawings and other works shall be
- 4.** done individually.
आवश्यक गणना, आरेखन एवं अन्य कार्य व्यक्तिगत रूप से किये
जायेंगे।

P.T.O

1. Verify application of superposition theorem in dc circuits.

2. Verify of kirchhoff's current Law and Kirchhoff's voltage Law in a dc circuit.

3. Study a four point manual starter of a dc motor.

4. Study the speed control of DC shunt motor by armature control method.

5. Study a three phase slip - ring induction motor.

6. To study and plot Forward and Reverse biased characteristics of Zener diode.

7. To study Two stage RC coupled amplifier.

8. To draw the characteristic curve of diode with respect to current.

9. To draw the characteristic curve of Zener diode.

10. To draw the characteristic curve of diode with respect to voltage.