

B.Tech 3rd Semester Exam., 2020
(New Course)

ANALOG ELECTRONIC CIRCUITS

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.
- (v) Symbols and notations carry their usual meanings.

1. Answer any seven questions of the following :

2×7=14

- (a) What is the function of clamping circuits?
- (b) Explain diode positive shunt clipper circuit with waveforms.
- (c) Write the important characteristics of common source configuration of JFET.

(d) Explain the half-wave rectifier with suitable diagram.

(e) What is integrator circuit?

(f) Write down the three differences between BJT and JFET.

(g) Explain the important characteristics of Darlington emitter-follower.

(h) What is precision rectifier circuit?

(i) What are the advantages of h-parameters?

Answer any four questions. Attempt any two parts from each :

2. (a) Derive the expression for stability factor for fix bias circuit with respect to I_{CO} , V_{BE} and β .
- (b) State and prove Miller's theorem.
- (c) A voltage divider biased circuit has $R_1 = 39\text{ k}\Omega$, $R_2 = 82\text{ k}\Omega$, $R_C = 3.3\text{ k}\Omega$, $R_E = 1\text{ k}\Omega$ and $CC = 18\text{ V}$. The silicon transistor has used $\beta = 120$. Find Q-point and stability factor. 7×2=14

3. (a) An op-amp has gain bandwidth product of 15 MHz. Determine the bandwidth of op-amp when $A_{CL} = 500$. Also, find the maximum value of A_{CL} when frequency is 200 KHz.
- (b) What are the advantages and features of instrumentation amplifier? Derive the expression for output voltage of instrumentation amplifier.
- (c) The data sheet of *N*-channel JFET gives the following details :
- $I_{DSS} = 9\text{mA}$ and pinch-off
voltage = -4.5V
- (i) At what value of V_{GS} will I_D be equal to 3 mA?
- (ii) What is its g_m at this I_D ? $7 \times 2 = 14$
4. (a) Derive an expression for input impedance voltage gain, current gain and output impedance for an emitter-follower circuit using *h*-parameter model for the transistor.

- (b) Explain the need of cascading amplifier. Draw and explain the block diagram of two-stage cascade amplifier.
- (c) Derive an expression for frequency of oscillators in Wien bridge oscillator.
- $7 \times 2 = 14$
5. (a) Explain the principle of operation of oscillator and effect of loop gain ($A\beta$) on the output of oscillator.
- (b) With the help of neat diagram, explain the construction working and characteristics of *N*-channel depletion-type MOSFET.
- (c) A given amplifier arrangement has the following voltage gains :
- $A_{v1} = 10, A_{v2} = 20$ and $A_{v3} = 40$
- Calculate the overall voltage gain and determine the total voltage gain in dB.
- $7 \times 2 = 14$

6. (a) Determine Z_{in} , Z_{out} and A_v for JFET common source amplifier with fixed bias configuration using AC equivalent small signal model.
- (b) With the help of neat diagram, explain the construction working and characteristics of N -channel JFET.
- (c) Explain the low frequency response of single-stage RC-coupled amplifier. $7 \times 2 = 14$
7. (a) Obtain an h -parameter equivalent circuit of CB and CE configurations.
- (b) With the help of block diagram, explain the concept of feedback.
- (c) Discuss with the help of circuit example, the purpose of providing—
 (i) negative feedback;
 (ii) positive feedback in amplifier. $7 \times 2 = 14$
8. (a) Draw the high frequency equivalent circuit of an emitter follower and derive the expression of upper cut-off frequency f_H .

- (b) Transistor's short circuit current gain is measured to be 25 at a frequency of 2 MHz. If $f_B = 200$ kHz, calculate the following :
- (i) The current gain bandwidth product
- (ii) h_{fe} at low frequency
- (iii) Short circuit current gain at 10 MHz and 100 MHz
- (c) A phase-shift oscillator uses three identical R - C sections in feedback network. The value of components are $R = 100 \text{ k}\Omega$ and $C = 0.01 \mu\text{F}$. Calculate the frequency of oscillator. $7 \times 2 = 14$
9. (a) An amplifier has a voltage gain of 40. The amplifier is now modified to provide a 10% negative feedback in series with the input. Determine the following :
- (i) Voltage gain with feedback
- (ii) Amount of feedback in dB
- (iii) Loop gain

- (b) Write the important advantage of a negative feedback amplifier and show that how bandwidth of an amplifier increases with negative feedback.
- (c) What is transistor biasing? Explain emitter bias circuit with relevant circuit and equations. 7×2=14
