

B.Tech 3rd Semester Exam., 2020
(New Course)

BASIC ELECTRONICS ENGINEERING

Time : 3 hours

Full Marks : 70

Instructions :


- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer the following questions (any seven) :

2×7=14


- (a) Why is negative feedback desired in amplifier application?
- (b) Draw the voltage transfer curve of op-amp.
- (c) State the Barkhausen's criteria for electronic system to oscillate with feedback.

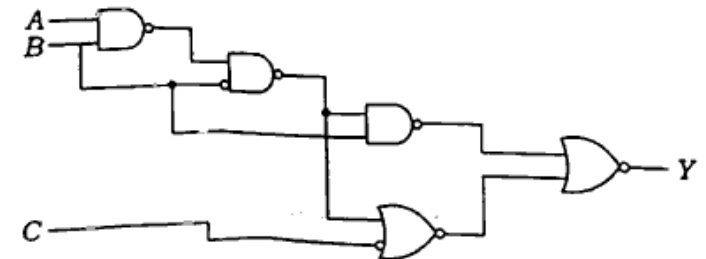- (d) How is amplifier different from the oscillator?
- (e) Why is the reception in the case of amplitude modulation usually noisy?
- (f) What is cell splitting and how does it increase the capacity of cellular network?
- (g) Justify that BJT is current controlled while FET is voltage-controlled device.
- (h) Name the breakdown mechanism in the lightly doped P-N junction diode under reverse biased condition.
- (i) Why is Gray code also called as reflected code? Convert $(396)_{10}$ to Gray code.
- (j) For the logical circuit shown in the figure below, derive the simplified Boolean expression for output Y :




(3)

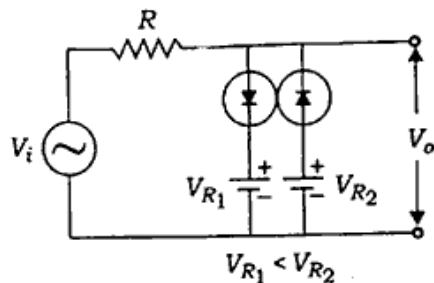2. (a) Draw the waveform of output V_o and explain the operation of circuit in the figure given below : 7




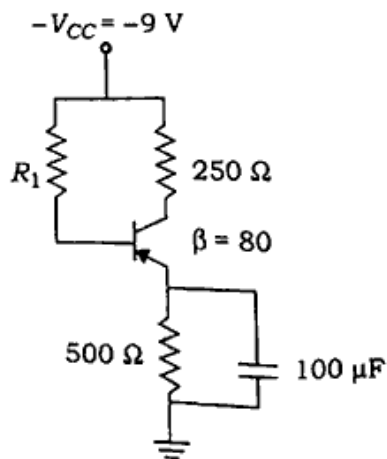- (b) Calculate the value of R_1 in the biasing circuit in the figure given below, so that the Q-point is fixed at $I_C = 8 \text{ mA}$ and $V_{CE} = 3 \text{ V}$: 7




(4)

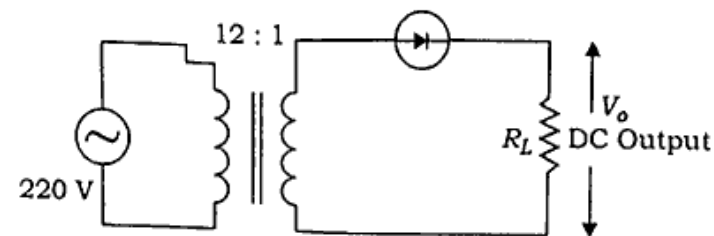3. (a) Calculate the maximum DC voltage and DC current available from a half-wave rectifier shown in the figure given below : 7



What is the PIV of the diode used in the rectifier? 7

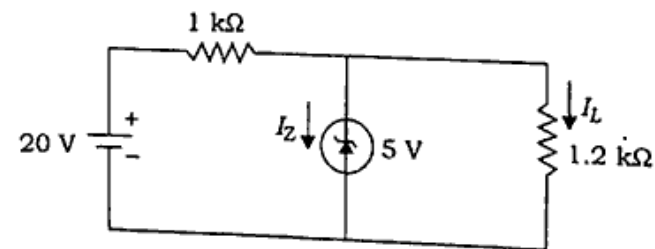- (b) In the figure given below, calculate the load current I_L and Zener diode current I_Z : 7




4. (a) Minimize the given Boolean function F using K map in SOP and implement using NAND gate : 7

$$F(A, B, C, D) = ABC\bar{D} + \bar{A}BCD + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D} + A\bar{C} + A\bar{B}C + \bar{B}C$$

(5)

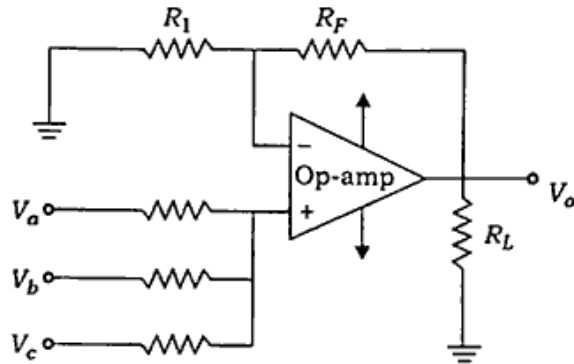- (b) The circuit given below is the basic application of op-amp to perform the addition operation :



Explain the operation of circuit and derive the expression of output voltage. 7

5. (a) Design the voltage follower using op-amp and explain the operation. 7
- (b) Draw the circuit diagram of voltage-shunt feedback amplifier and derive the expression of closed-loop voltage gain. 7
6. (a) Draw the block diagram of cellular network and briefly explain its operation. 7
- (b) Draw the functional block diagram of AM transmitter and receiver. 7
7. (a) Design Schmitt trigger using IC 555 timer and explain its operation with the help of functional diagram. 7

(6)

- (b) If $R_1 = R_2 = R_3 = 450 \text{ k}\Omega$ and $C_1 = C_2 = C_3 = 60 \text{ pF}$, determine the frequency of oscillation in phase-shift oscillator. Draw the basic circuit of an R-C phase-shift oscillator and explain its operation. 7

8. (a) A new clocked X-Y flip-flop is defined with inputs X and Y in addition to the clock input. The flip-flop functions are as follows :

If $XY = 00$, the flip-flop changes state with each clock pulse. If $XY = 01$, the flip-flop state Q becomes 1 with the next clock pulse. If $XY = 10$, the flip-flop state Q becomes 0 with the next clock pulse. If $XY = 11$, no change of state occurs with the clock pulse.

Write the truth table and excitation table of X-Y flip-flop. Implement the X-Y flip-flop using a J-K flip-flop. 7

- (b) What is the race around condition in J-K flip-flop? What are the methods to resolve the race around condition in J-K flip-flop? Explain each method with the help of example. 7

9. (a) What are the problems with normal encoder? How can these problems be solved by the priority decoder? Design 2 to 4 lines priority encoder. 7
- (b) Draw the block diagram of micro-controller and briefly explain each block. 7
