

Code : PCC-EEE-01 (100306)

(2)

B.Tech 3rd Semester Special Exam., 2020

ELECTRICAL CIRCUIT ANALYSIS

Time : 3 hours

Full Marks : 70

Instructions:

- (i) The marks are indicated in the right-hand margin.
- (ii) There are NINE questions in this paper.
- (iii) Attempt FIVE questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer any seven questions of the following : 2x7=14

(a) Find the current I in the circuit of Fig. 1 by using the superposition theorem :

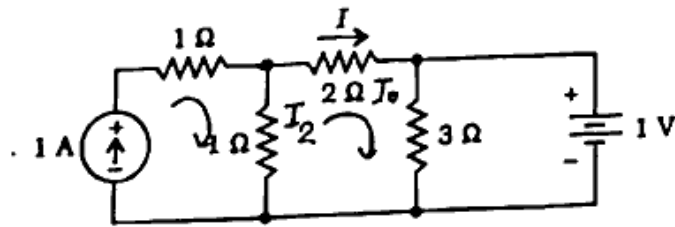


Fig. 1

(Turn Over)

(b) In Fig. 2, find the value of R_{Th} and I_{SC} :

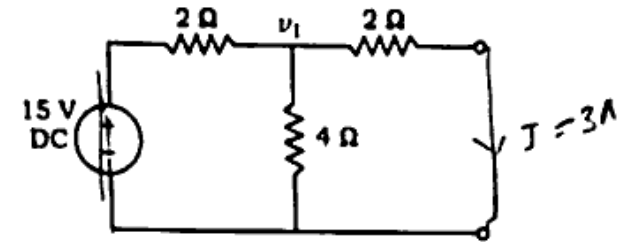


Fig. 2

(c) Find the value of R_L of Fig. 3 so that the maximum power can be transferred :

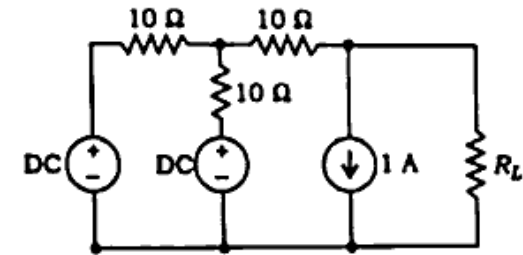


Fig. 3

(d) Find the Z-parameters of the two-port network shown in Fig. 4 :

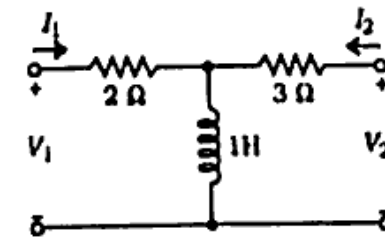


Fig. 4

(Continued)

(4)

- (i) Two coupled coils have self-inductances $L_1 = 50 \text{ mH}$ and $L_2 = 200 \text{ mH}$, and a coefficient of coupling $k = 0.5$. If coil 2 has 1000 turns, and $i_1 = 5.0 \sin 400t \text{ A}$, find the voltage at coil 2.

2. (a) Use the superposition theorem in the circuit shown in Fig. 7 to find current I : 7

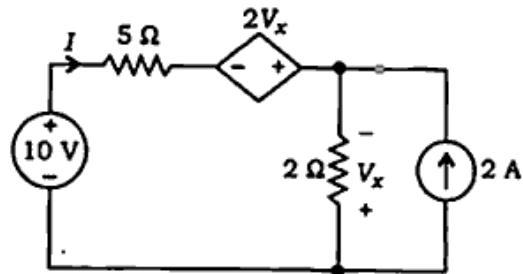


Fig. 7

- (b) Draw the Thévenin's equivalent circuit of Fig. 8 and hence find the current through $R = 2\Omega$. (All the resistances shown in the figure are in ohm): 5

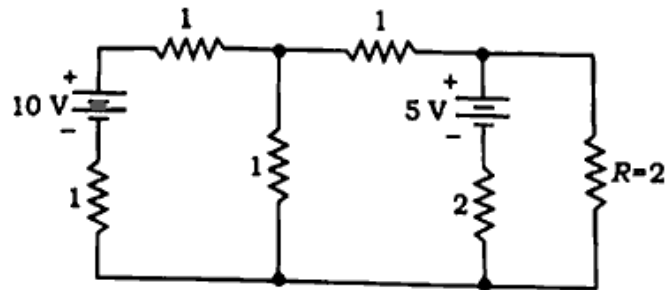


Fig. 8

(5)

- (c) State compensation theorem. 2

3. (a) Find the current I_0 of Fig. 9 using the superposition theorem: 5

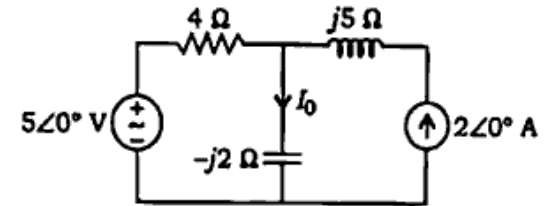


Fig. 9

- (b) In the circuit of Fig. 10, find the effective value of the resistance seen by the source V_s : 3

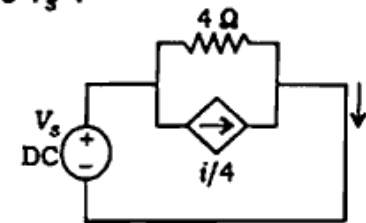


Fig. 10

- (c) Define incidence matrix. Find the complete incidence matrix of the graph shown in Fig. 11: 2+4=6

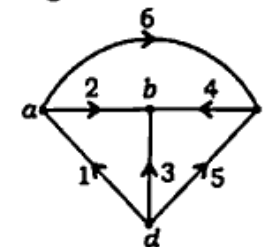


Fig. 11

4. (a) Define the g -parameters of an electrical circuit. 2
- (b) Find the g -parameters in the circuit shown in Fig. 12 : 5

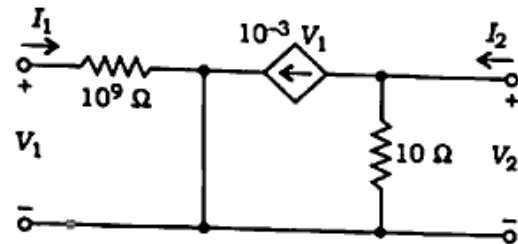


Fig. 12

- (c) Find the Z -parameters and Y -parameters of the circuit shown in Fig. 13 : 7

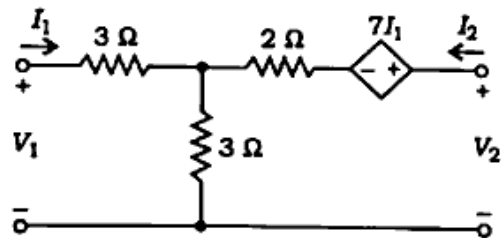


Fig. 13

5. (a) Find the Laplace transform of $f(t) = e^{-at} \cos(\omega t)$, $a > 0$. 4
- (b) Calculate the inverse Laplace transform of $F(s) = \frac{1}{s(s^2 - a^2)}$. 5

- (c) In the series R - C circuit, the capacitor has an initial charge 2.5 mC . At $t=0$, the switch is closed and a constant-voltage source $V = 100 \text{ V}$ is applied. Use the Laplace transform method to find the current in the circuit after closing the switch. 5

6. (a) Draw the graph for the given incidence matrix : 4

$$[A] = \begin{bmatrix} -1 & 0 & 0 & 0 & 1 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & -1 & -1 & 0 & -1 & 0 & -1 \\ 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 1 & 1 & 1 & 1 & 0 & 0 & 0 & 0 \end{bmatrix}$$

- (b) Find the cut-set matrix from the graph as shown in Fig. 14 : 5

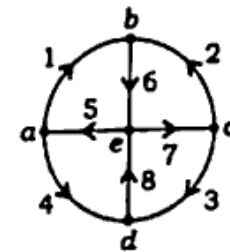


Fig. 14

- (c) Consider the network shown in Fig. 15, draw the graph and determine (i) number of links, (ii) rank of the graph and (iii) total number of trees : 5

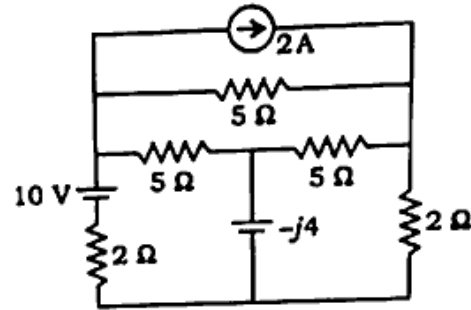


Fig. 15

7. (a) State the characteristics of an ideal transformer. 2
- (b) Define r.m.s. value from factor, peak factor, complex power and half power frequency. 5
- (c) Calculate the resonant frequency of a series R-L-C circuit. 3
- (d) Obtain the current in each branch of the network shown in Fig. 16, using the mesh current method : 4

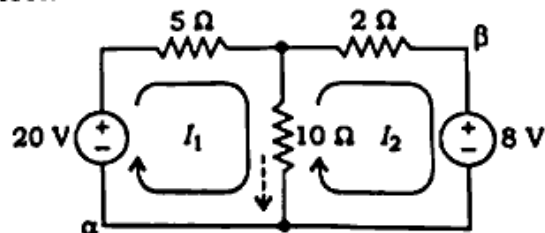


Fig. 16

8. (a) Obtain the total power supplied by the 60 V source and the power absorbed in each resistor in the network of Fig. 17 : 7

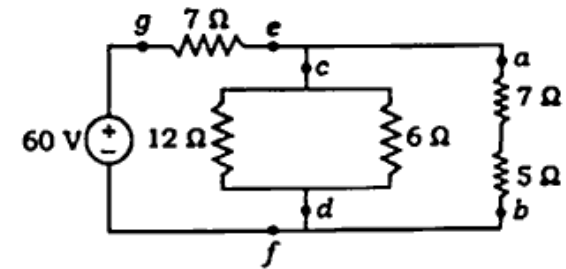


Fig. 17

- (b) Compute the mesh currents of Fig. 18 : 5

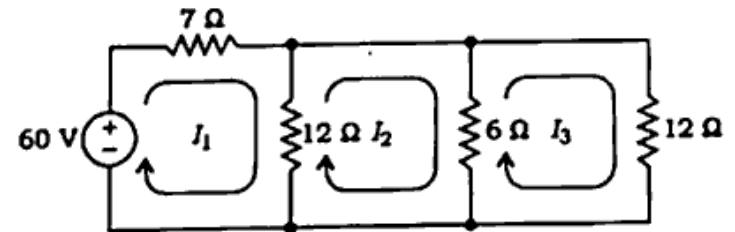


Fig. 18

- (c) Define supermesh and supernode. 2
9. (a) Derive step response of a series R-C circuit. 5
- (b) Define forced response and natural response. 2

(10)

- (c) For the circuit shown in Fig. 19, the switch K is moved from position 1 to position 2 at $t = 0$ s. Find the current $i(t)$ assuming $i(0_+) = 2$ A and $V_c(0_+) = 2$ V : 7

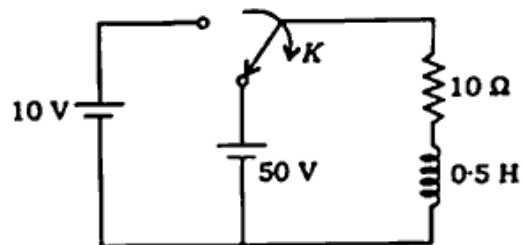


Fig. 19
