

Code : ESC-202 (101302)

**B.Tech 3rd Semester Special  
Exam., 2020  
( New Course )**

**BASIC ELECTRONICS**

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer/Fill in the blanks/Write true or false  
(any seven) :  $2 \times 7 = 14$
- (a) Why is filter required to be added after rectifier circuit?
  - (b) What is the application of voltage regulator?
  - (c) DC value of pure AC waveform is \_\_\_\_\_.

20AK/1302

( Turn Over )

- (d) Which of the transistor currents is always the largest?
  - (e) What is the source of leakage current in a transistor?
  - (f) What is the major difference between a bipolar and a unipolar device?
  - (g) Give the advantage of negative feedback in amplifier.
  - (h) BJT amplifier changes the frequency and shape of the signal.
  - (i) CMMR for ideal operational amplifier is \_\_\_\_\_.
  - (j) Slew rate for ideal operational amplifier is \_\_\_\_\_.
2. (a) Draw volt-ampere characteristics of a Zener diode. What is meant by the knee voltage in the curve?
- (b) Describe in detail the avalanche breakdown mechanism in a diode.  $6+8=14$
3. (a) Explain the principle of operation of LED with the help of diagram.
- (b) Derive the expression for  $I_C$  in terms of  $I_E$  and  $\alpha_{dc}$  for a common-base BJT configuration. For a given  $\alpha_{dc}$  of 0.998, determine  $I_C$  if  $I_E = 4$  mA.  $6+8=14$

20AK/1302

( Continued )

4. (a) Define the stability factor. What does smaller stability factor indicate?  
(b) Derive the expression for stability factor for voltage divider bias (self-bias) circuit. 5+9=14
5. (a) Explain the construction and characteristics of FET.  
(b) Draw and explain *h*-parameter small signal model for BJT. 7+7=14
6. (a) Explain the working of common emitter amplifier with the help of circuit diagram. <https://www.akubihar.com>  
(b) What are the roles of coupling and bypass capacitors? Explain in detail. 8+6=14
7. (a) Describe the RC phase-shift oscillator with circuit diagram.  
(b) Explain the working of high-frequency LC oscillator with the help of circuit diagram. 6+8=14
8. (a) Explain the working of voltage series feedback amplifier with the help of block diagram.  
(b) Design an integrator using op-amp and explain its working. 7+7=14

9. (a) Write the circuit diagram of differential amplifier configurations and explain its working.  
(b) Explain about CMRR, slew rate and concept of virtual ground. 7+7=14

\*\*\*