

Code : 100101

(2)

B.Tech 1st Semester Exam., 2018 (New)

BASIC ELECTRICAL ENGINEERING

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

1. Answer any seven short answer-type questions : 2×7=14

- (a) Introduce resistance, inductance and capacitance.
- (b) State superposition theorem.
- (c) A sinusoidal voltage of 60 Hz has a maximum value of $100\sqrt{2}$ volts. At what time measured from a positive maximum value will the instantaneous voltage be 100 volts?

- (d) What are the two main advantages of DC excitation system?
- (e) In two-wattmeter method, what will be the power factor when both wattmeters show 50 watts readings?
- (f) Explain power triangle.
- (g) How do hysteresis and eddy current loss depend on frequency?
- (h) Define average value and RMS value.
- (i) Explain generation of rotating magnetic field in electrical machine.
- (j) Differentiate among neutral, grounding and earthing.

2. (a) Find R to have maximum power transfer in the circuit shown in Fig. 1. Also obtain the amount of maximum power : 6

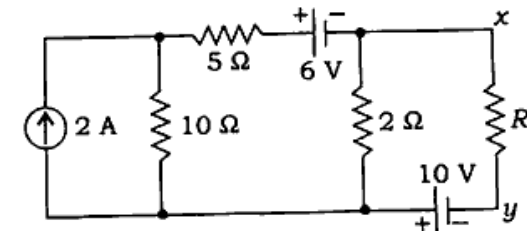



Fig. 1

- (b) A coil having resistance of $10\ \Omega$ and inductance of $1\ \text{H}$ is switched on to a direct voltage of $100\ \text{V}$. Calculate the rate of change of the current (i) at the instant of closing the switch and (ii) when $t = L/R$. Also find the steady-state value of the current. 8
3. (a) What is the phase relationship between R , L and C components in a series AC circuit? What are active power, reactive power and apparent power? 6
- (b) On a power distribution system, three loads run in parallel :
- Load A : $100\ \text{VA}$, $0.5\ \text{pf}$ (lag)
- Load B : $150\ \text{W}$, $0.8\ \text{pf}$ (lead)
- Load C : $200\ \text{VA}$, $100\ \text{var}$ (lag)
- Find the net power position. 8
4. (a) What is eddy-current loss? What are the undesirable effects of eddy currents? How can they be minimized? Mention some applications of eddy-currents. 6

- (b) An iron ring of cross-sectional area $5\ \text{cm}^2$ is wound with a wire of 120 turns and has a cut of $3\ \text{mm}$. Calculate the magnetizing current required to produce a flux of $0.3\ \text{m Wb}$, if mean length of magnetic path is $25\ \text{cm}$ and relative permeability of iron is 650. 8
5. (a) Define voltage regulation of a transformer and derive conditions for (i) zero regulation and (ii) maximum regulation. Also draw the curve of variation of voltage regulation with power factor. 6
- (b) Derive an expression for the induced e.m.f. of a transformer. A $3000/200\ \text{V}$, $50\ \text{Hz}$, single-phase transformer is built on a core having an effective cross-sectional area of $150\ \text{cm}^2$ and has 80 turns in the low-voltage winding. Calculate—
- (i) the value of the maximum flux density in the core;
- (ii) the number of turns in the high-voltage winding. 8

(5)

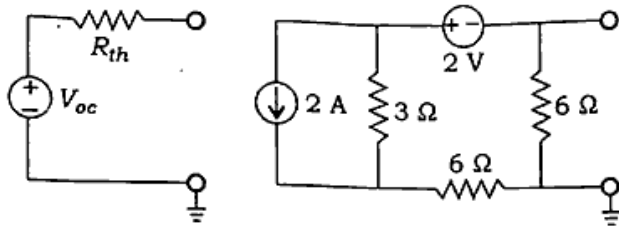6. The circuit shown in Fig. 2(i) is the Thevenin equivalent circuit of the circuit shown in Fig. 2(ii). Find the value of the open circuit voltage, V_{oc} and Thevenin resistance, R_{th} . 14



<http://www.akubihar.com>

Fig. 2 (i)

Fig. 2 (ii)

7. Determine current in 12 Ω resistance using Norton's theorem in the network shown in Fig. 3 : 14

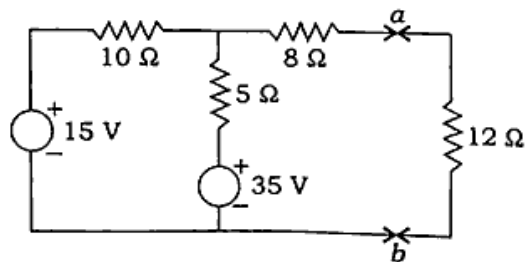


Fig. 3

(6)

8. A 100 MVA Y-connected 13.2 kV synchronous generator is connected to a 13.2/132 kV, 100 MVA delta-star transformer. The generators are $X''_d = 0.1$ pu, $X'_d = 0.25$ pu, $X_d = 1.2$ pu on a 100 MVA base, while transformer reactance is 0.1 pu on the same base. The machine is operating on no load, at rated voltage when a three-phase fault occurs at the HT terminals of transformer. Determine—

- the sub-transient, transient and steady-state symmetrical fault currents in pu and amperes;
 - the maximum possible DC component;
 - the maximum value of instantaneous current.
9. (a) Derive the expressions of equivalent star network resistances from the delta network comprising of R_{12} , R_{23} , R_{31} , where nodes are termed as 1, 2 and 3 respectively. 7

(7)

(b) What is the main purpose of providing taps in transformer? Suggest the addition in a simplified transformer model when it is used for tap changing transformer.

7
